

d) See Topic: MEMORY DEVICE, Long Answer Type Question No. 1.

QUESTION 2005

1. Answer all questions:

- a) Determine decimal equivalent for $(1011.101)_2$.
 - b) What do you mean by tristate logic gate?
 - c) Represent 38 in 1's complement representation for a 8-bit word.
 - d) Design a 2-input XOR gate using 2-input NOR gate.
 - a) See Topic: NUMBER SYSTEM, Short Answer Type Question No. 4.
 - b) See Topic: LOGIC GATES, Short Answer Type Question No. 2.
 - c) See Topic: NUMBER SYSTEM, Short Answer Type Question No. 1.
 - d) See Topic: BOOLEAN ALGEBRA, Short Answer Type Question No. 1.
- e) Draw a module 2 counter circuit using basic gates.

- f) Difference between Binary code and Gray code.
 - g) How is demultiplexer used as a data distributor?
 - h) Determine 8's complement of $(47.23)_8$.
 - i) Subtract 10110 from 01011 using 2's complement method and state the sign of the result.
 - f) See Topic: CODES, Short Answer Type Question No. 1.
 - g) See Topic: COMBINATIONAL CIRCUIT, Long Answer Type Question No. 3(a).
 - h) See Topic: NUMBER SYSTEM, Short Answer Type Question No. 2.
 - i) See Topic: NUMBER SYSTEM, Short Answer Type Question No. 3.
2. a) Prove the following Boolean functions:
- i) $x + \overline{xy} = x + y$
 - ii) $\overline{cd + a + a + cd + ab} = a + cd$
- b) A 5-input NAND gate has one logic 0 input which is fed to 4-input NOR gate with one logic input. Explain the output in detail.
See Topic: BOOLEAN ALGEBRA, Long Answer Type Question No. 3.
3. a) Define excitation table? Derive the excitation table for RS flip-flop. What do you mean by forbidden inputs?
- b) Design a 4 to 1 line multiplexer using basic logic gates.
a) See Topic: FLIP-FLOP, Long Answer Type Question No. 3.
b) See Topic: COMBINATIONAL CIRCUIT, Long Answer Type Question No. 3(b).
4. Design and explain the logic diagram of a Master-Slave JK flip-flop using NAND gates only.
See Topic: FLIP-FLOP, Long Answer Type Question No. 2(a).
5. Distinguish between JK flip-flop and SR flip-flop with their logic diagrams and truth table.
See Topic: FLIP-FLOP, Long Answer Type Question No. 4.
6. Derive a Binary to Gray code converter and write down the truth table.
See Topic: KARNAUGH MAP, Long Answer Type Question No. 1.
7. a) Sketch a parity checker circuit for a 5-bit word. Explain with example for odd and even parity.
- b) Using K-map method to obtain the minimized form for the following function:

$$f(A, B, C, D) = \sum (0, 2, 3, 6, 7, 12, 13, 14) + \sum d.c. (1, 4, 11, 15)$$
- c) Why is Gray code used in K-map minimization?
- d) Convert JK flip-flop to T and D flip-flop.
- e) Application of XS-3 code with example.
- f) Design a circuit of Gray to Binary code converter for 5-bit word.
a) See Topic: COMBINATIONAL CIRCUIT, Long Answer Type Question No. 4.
b) See Topic: KARNAUGH MAP, Short Answer Type Question No. 2.
c) See Topic: KARNAUGH MAP, Short Answer Type Question No. 3.
d) See Topic: FLIP-FLOP, Short Answer Type Question No. 2.
f) See Topic: CODES, Long Answer Type Question No. 1.

POPULAR PUBLICATIONS

8. Write short notes of the following:

- a) Shift register.
- b) Dynamic RAM
- c) ~~Tristate logic~~
- d) Open collector gate

- a) See Topic: RESISTER & COUNTER, Long Answer Type Question No. 10(a).
- b) See Topic: MEMORY DEVICE, Long Answer Type Question No. 3(b).
- d) See Topic: LOGIC GATES, Long Answer Type Question No. 4(a).

qapaper