

QUESTION 2009

Group - A

(Multiple Choice Type Question)

1. Chose the correct alternatives for the following:

- i) A 3-bit synchronous counter uses flip-flops with propagation delay time of 20 ns each. The maximum possible time required for change of state will be
a) 60 ns b) 40 ns ✓ c) 20 ns d) none of these
- ii) BCD subtraction is performed by using which complement representation?
a) 1's b) 2's c) 10's ✓ d) 9's
- iii) The SOP form of logical expression is most suitable for designing logic circuits using only
a) XOR gates b) NOR gates ✓ c) NAND gates d) OR gates
- iv) The dual of a Boolean function is obtained by
a) interchanging all 0s and 1s only
b) changing 0s to 1s only
c) changing 1s to 0s only
✓ d) interchanging all 0s and 1s and '+' and '.' signs
- v) When representing in the following code the consecutive decimal number differ only in one bit
a) Excess -3 ✓ b) Gray c) BCD d) Hexadecimal
- vi) In a J-K flip-flop when $J = 1$ and $K = 1$ and clock = 1 the output will be.
✓ a) toggle b) 1 c) 0 d) recalls previous output
- vii) $(AB + A'B + AB')$ is equal to
a) $A+B'$ ✓ b) $A'+B$ c) $A+B$ d) 1
- viii) 2's complement of 1010101 is
✓ a) 0101011 b) 10101010 c) 1100000 d) 1000001

BCA DE-123

POPULAR PUBLICATIONS

ix) The basic fuse technologies used in PROM are

a) metal links

b) silicon links

c) p-n junctions

✓ d) all of these

x) In general, a boolean expression of $(n+1)$ variable can be implemented using a multiplexer with

✓ a) 2^{n+1} inputs

b) 2^{n-1} inputs

c) 2^n inputs

d) None of these

Group – B

(Short Answer Type Questions)

2. Draw the neat diagram of 3- bits Bi-directional Shift Register using mode control (M). When M is logic zero then left shift and right shift for M is logic one.

See Topic: REGISTER & COUNTER, Long Answer Type Question No. 6.

3. Design 2-bit Gray-Binary converter using basic logic gates with proper truth table.

See Topic: COMBINATIONAL CIRCUIT, Long Answer Type Question No. 8.

4. Draw the logic diagram and truth table of J – K F/F. Why is J- K F/F much more versatile than S-R F/F?

See Topic: FLIP-FLOP, Long Answer Type Question No. 10.

5. What is a full subtractor? Explain its basic structure with proper logic diagrams & truth table.

See Topic: ARITHMETIC CIRCUIT, Long Answer Type Question No. 3.

6. Realize the function $f(A, B, C) = \sum m(1, 3, 5, 6)$ by a multiplexer. Discuss the operation logic.

See Topic: LOGIC GATES, Short Answer Type Question No. 4.

Group – C

(Long Answer Type Questions)

7. a) Using K-map method minimize the following expression:

$$F(w, x, y, z) = \sum m(1, 5, 6, 12, 13, 14) + d \sum (2, 4).$$

b) Implement Ex-OR gate using NAND Gate and NAND gate using NOR gate.

a) See Topic: KARNAUGH MAP, Short Answer Type Question No. 6.

b) See Topic: LOGIC GATES, Short Answer Type Question No. 4.

8. a) Design and implement Mod-6 synchronous counter considering lock out problem. Is the counter self-starting?

b) Explain the difference between Ring and Johnson Counter with proper state diagram and circuit diagram.

See Topic: REGISTER & COUNTER, Long Answer Type Question No. 7.

9. a) Explain the concept of parity checking.

b) Discuss about the design of an odd parity generator.

a) See Topic: COMBINATIONAL CIRCUIT, Long Answer Type Question No. 8(a).

b) See Topic: COMBINATIONAL CIRCUIT, Long Answer Type Question No. 4.

c) What is biased Representation (FPR)?

d) Represent for a 32-bit CPU.

DIGITAL ELECTRONICS

10. What do you mean by race condition in flip-flop? Design a j-k flip-flop and discuss its operation. Design and explain the functioning of the 4-bit adder-subtractor circuit.

See Topic: FLIP-FLOP, Long Answer Type Question No. 11.

See Topic: ARITHMETIC CIRCUIT, Short Answer Type Question No. 2.

11. Write short notes on any three of the following:

- a) Universal gates
- b) Decoder
- c) Shift Register
- d) Flip-flop excitation table
- e) Ripple counter

a) See Topic: LOGIC GATES, Long Answer Type Question No. 4(b).

b) See Topic: COMBINATIONAL CIRCUIT, Long Answer Type Question No. 14(f).

c) See Topic: RESISTER & COUNTER, Long Answer Type Question No. 10(a).

d) See Topic: FLIP-FLOP, Long Answer Type Question No. 13(a).

e) See Topic: RESISTER & COUNTER, Long Answer Type Question No. 10(e).